

计算机组成原理大作业——设计实现控制单元 CU

1120310xxx xxxx

微程序设计控制单元的主要任务是编写对应各条机器指令的微程序，具体步骤是首先写出对应机器指令的全部微操作及节拍安排，然后确定微指令格式，最后编写出每条微指令的二进制代码（称为微指令码点）。

写出对应机器指令的微操作及节拍安排

不考虑简介寻址和中断的情况。下面分别按取指阶段和执行阶段列出其微操作序列。

(1) 取指阶段的微操作及节拍安排

T0 PC→MAR, 1→R
T1 M(MAR)→MDR, (PC)+1→PC
T2 MDR→IR, OP(IR)→微地址形成部件（编码器：指令码→微地址）（此步为组合逻辑，自动完成，不需要控制信号）

(2) 执行阶段的微操作及节拍安排

执行阶段的微操作由操作码性质而定，同时也需要考虑下地址的形成问题。

1) CLA 指令

T0 0→AC

2) COM 指令

T0 ~AC→AC

3) SHR 指令

T0 L(AC)→R(AC), AC0→AC0

4) CSL 指令

T0 R(AC)→L(AC), AC0→ACn

5) STP 指令

T0 0→G

6) ADD 指令

T0 Ad(IR)→MAR, 1→R

T1 M(MAR)→MDR

T2 (AC)+(MDR)→AC

7) STA 指令

T0 Ad(IR)->MAR, 1->W

T1 AC->MDR

T2 MDR->M(MAR)

8) LDA 指令

T0 Ad(IR)->MAR, 1->R

T1 M(MAR)->MDR

T2 MDR->AC

9) JMP 指令

T0 Ad(IR)->PC

10) BAN 指令

T0 $A0 * Ad(IR) + \sim A0 * (PC) \rightarrow PC$

确定微指令格式

微指令的格式包括微指令的编码方式、下地址的形成方式和指令字长 3 方面。

(1) 微指令的编码方式

直接编码。具体如下表。

第 0 位表示控制 PC->MAR

第 1 位表示控制 1->R

第 2 位表示控制 M(MAR)->MDR

第 3 位表示控制 (PC)+1->PC

第 4 位表示控制 MDR->IR

第 5 位表示控制 0->AC

第 6 位表示控制 $\sim AC \rightarrow AC$

第 7 位表示控制 L(AC)->R(AC), AC0->AC0

第 8 位表示控制 R(AC)->L(AC), AC0->ACn

第 9 位表示控制 0->G

第 10 位表示控制 Ad(IR)->MAR

第 11 位表示控制 (AC)+(MDR)->AC

第 12 位表示控制 1->W

第 13 位表示控制 AC->MDR

第 14 位表示控制 MDR->M(MAR)

第 15 位表示控制 MDR->AC

第 16 位表示控制 Ad(IR)->PC

第 17 位表示控制 $A0 * Ad(IR) + \sim A0 * (PC) \rightarrow PC$

(2) 下地址形成方式

采用微指令的下地址字段和指令的操作码编码两种形成方式。设置一控制位，0 表示前一种方式，1 表示后一种方式，作为二路数据选择器的控制端输入。

第 18 位表示控制下地址形成方式 0 表示选择顺序控制字段 1 表示选择操作码编码结果

(3) 微指令字长

假设模型机存储字长和指令字长均为 16 位，地址字长为 8 位。采用 16 位定长指令，操作码为前 5 位,中间 3 位保留，地址码为后 8 位。

指令系统如下：

指令助记符	操作数	指令码	长度
CLA		02H	2；累加器清零
COM		03H	2；累加器取反
SHR		04H	2；算数右移
CSL		05H	2；循环左移
STP		06H	2；停机
ADD	[*]	07H	2；加法
STA	[*]	09H	2；存数
LDA	[*]	0BH	2；取数
JMP	*	0DH	2；无条件跳转
BAN	*	0EH	2；负则转

18 个微操作，19 条微指令。不考虑指令系统的扩充，操作控制字段取 18 位（0~17），下地址控制字段取 1 位（18），顺序控制字段（下地址）取 5 位（19~23）。

编写微指令码点

表中空格中“0”省略。

对应 10 条机器指令的微指令码点

[illegible]

(4) 学习编写 testbench，同样也是找相似的代码，读懂，仿照着写出自己的测试要求。

(5) 元件调用。各模块编写完成后，通过百度学习元件调用的方法，从网上优秀课件中找到元件实例化的语法、用法，最终实现整个 CU 各模块的协同工作。

(6) 整个过程都反复的在看 VHDL 的系统讲解，一开始没有实例，系统讲解不知所云何物，随着在实例中碰到各种问题，再回过头看理论讲解，才不断有所收获。大约反复 5~7 遍，可以大体上了解 VHDL 语言的各个要素以及编写思想。

代码及仿真波形

代码

(1) 微地址形成部件

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity uaddr_gen is
    Port ( op : in  STD_LOGIC_VECTOR (4 downto 0);
          op_add : out  STD_LOGIC_VECTOR (4 downto 0));
end uaddr_gen;

architecture Behavioral of uaddr_gen is
begin
    process(op) begin
        op_add <= op(3 downto 0)&'0';
    end process;
end Behavioral;
```

(2) 5 位 2 选 1 多路选择器

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL, IEEE.NUMERIC_STD.ALL;

entity MUX is
    PORT(
        mode          :IN STD_LOGIC; --输入控制信号
        next_add :IN STD_LOGIC_VECTOR(4 DOWNTO 0); --5 位下地址数据端
        op_addr       :IN STD_LOGIC_VECTOR(4 DOWNTO 0); --5 位微程序入口地址数据端
        out_add       :OUT STD_LOGIC_VECTOR(4 DOWNTO 0)); --5 位下地址输出
end MUX;

architecture Behavioral of MUX is
    signal tmp          :STD_LOGIC;
    begin
        tmp <= mode;
        process(tmp,next_add,op_addr) begin
            case tmp is
                when '0' => out_add <= next_add;
                when others => out_add <= op_addr;
            end case;
        end process;
    end Behavioral;
```

(3) 控制存储器

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.std_logic_unsigned.ALL;          --CONV_INTEGER

entity ROM is
    Port ( add : in  STD_LOGIC_VECTOR (4 downto 0);
          data_out : out  STD_LOGIC_VECTOR (0 to 23));
end ROM;

architecture Behavioral of ROM is
    type microcode_array is array(28 downto 0) of std_logic_vector(0 to 23);
    constant code          : microcode_array:=
        0=> "11000000000000000000000001",
        1=> "00110000000000000000000010",
        2=> "00001000000000000001UUUUU",
        4=> "00000100000000000000000000",
        6=> "00000010000000000000000000",
```

```

        8=> "000000010000000000000000",
        10=> "000000001000000000000000",
        12=> "000000000100000000000000",
        14=> "010000000010000000001111",
        15=> "0010000000000000000010000",
        16=> "000000000001000000000000",
        18=> "000000000010100000010011",
        19=> "000000000000010000010100",
        20=> "00000000000001000000000",
        22=> "010000000010000000010111",
        23=> "001000000000000000011000",
        24=> "000000000000000100000000",
        26=> "000000000000000010000000",
        28=> "000000000000000001000000",
        others=>"0000000000000000000000");
begin
    data_out <= code(conv_integer(add));
end Behavioral;

```

(4) CMDR

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity CMDR is
    GENERIC(n : Positive := 24); --size of counter/shifter
    Port (
        clock : IN Std_logic; --serial inputs
        u_op : in STD_LOGIC_VECTOR (0 TO (n-1));
        control : out STD_LOGIC_VECTOR (0 TO 17);
        mode_sel: out STD_LOGIC;
        next_add : out STD_LOGIC_VECTOR (4 DOWNT0 0));
end CMDR;

architecture Behavioral of CMDR is
    SIGNAL int_reg : Std_logic_vector(0 TO 23);

    BEGIN
        main_proc : PROCESS
        BEGIN
            WAIT UNTIL rising_edge(clock);
            int_reg <= u_op;
        END PROCESS;
        --connect internal register to dataout port
        control <= int_reg(0 TO 17);
        mode_sel<= int_reg(18);
        next_add <= int_reg(19 TO 23);
    end Behavioral;

```

(5) 总的CU

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity CU is
    Port ( clk : in STD_LOGIC;
        op_code : in STD_LOGIC_VECTOR (4 downto 0);
        ctrl_signal : out STD_LOGIC_VECTOR (17 downto 0));
end CU;

architecture Behavioral of CU is

    component CMAR
        GENERIC(n : Positive := 24); --size of counter/shifter
        Port (
            clock : IN Std_logic; --serial inputs
            u_op : in STD_LOGIC_VECTOR (0 TO (n-1));
            control : out STD_LOGIC_VECTOR (0 TO 17);
            mode_sel: out STD_LOGIC;
            next_add : out STD_LOGIC_VECTOR (4 DOWNT0 0));
    end component;

    component uaddr_gen
        Port ( op : in STD_LOGIC_VECTOR (4 downto 0);
            op_add : out STD_LOGIC_VECTOR (4 downto 0));
    end component;

    component MUX
    PORT(
        mode :IN STD_LOGIC; --输入控制信号
        next_add:IN STD_LOGIC_VECTOR(4 DOWNT0 0); --5 位下地址数据端
        op_addr :IN STD_LOGIC_VECTOR(4 DOWNT0 0); --5 位微程序入口地址数据端
    
```

```

        out_add :OUT STD_LOGIC_VECTOR(4 DOWNTO 0)); --5 位下地址输出
end component;

component ROM
    Port ( add : in  STD_LOGIC_VECTOR (4 downto 0);
          data_out : out  STD_LOGIC_VECTOR (0 to 23));
end component;


signal op_add_MUX:std_logic_vector(4 downto 0);
signal mode_MUX :std_logic;
signal next_add_MUX:std_logic_vector(4 downto 0);
signal MUX_CM :std_logic_vector(4 downto 0);
signal CM_CMAR :std_logic_vector(0 to 23);

begin
u1:uaddr_gen port map(op_code, op_add_MUX);
u2:MUX      port map(mode_MUX, next_add_MUX, op_add_MUX, MUX_CM);
u3:ROM      port map(MUX_CM, CM_CMAR);
u4:CMAR     port map(clk, CM_CMAR, ctrl_signal, mode_MUX, next_add_MUX);
end Behavioral;

```


仿真波形

(1) 微地址形成部件

 

可以看出，op_add 是 op 左移一位的结果。


(2) 5 位 2 选 1 多路选择器

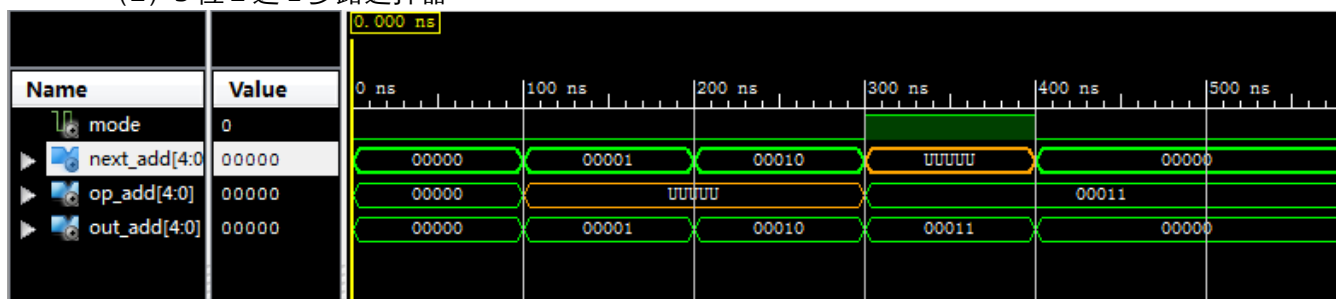


当 mode 为 0 时，out_add 输出 next_add，当 mode 为 1 时，out_add 输出 op_add。

(3) 控制存储器

下图——输出每条微指令。

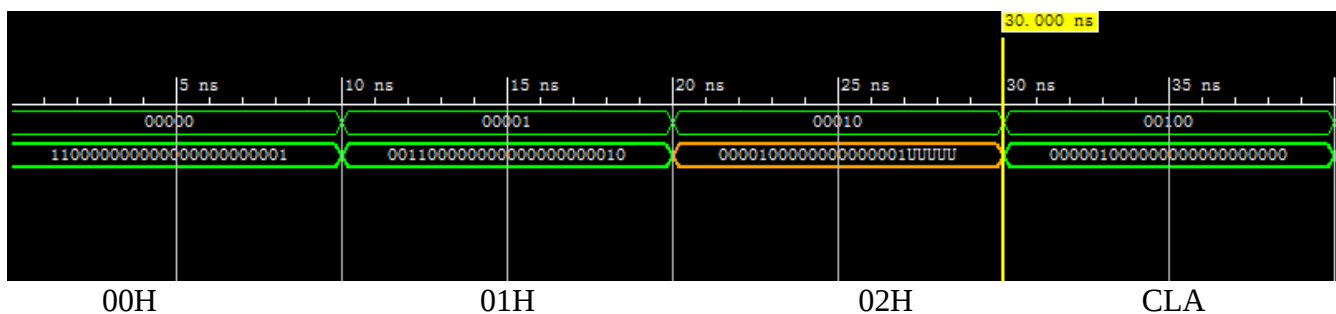

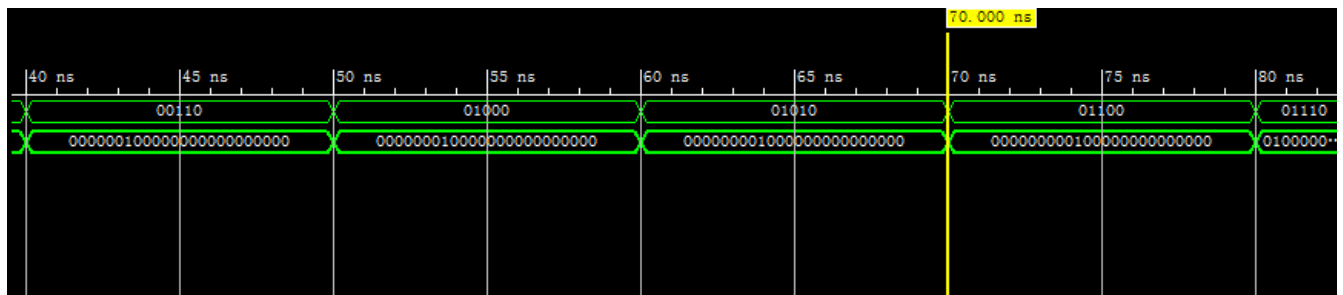


COM

SHR


CSL

STP

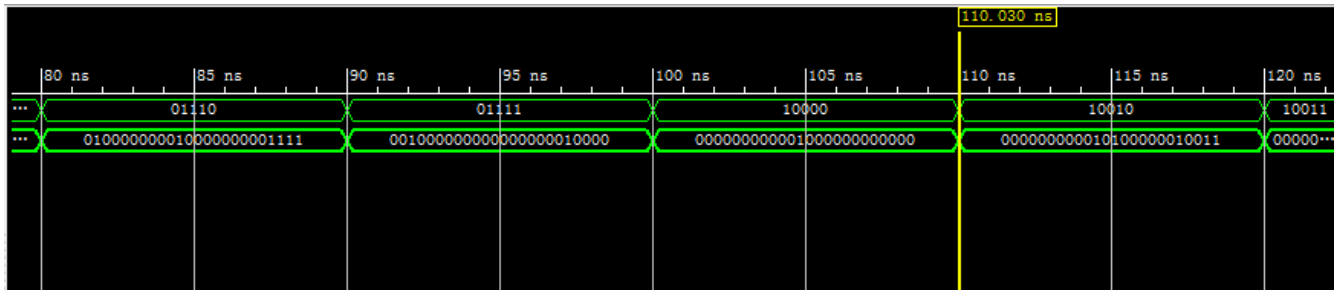


ADD

STA

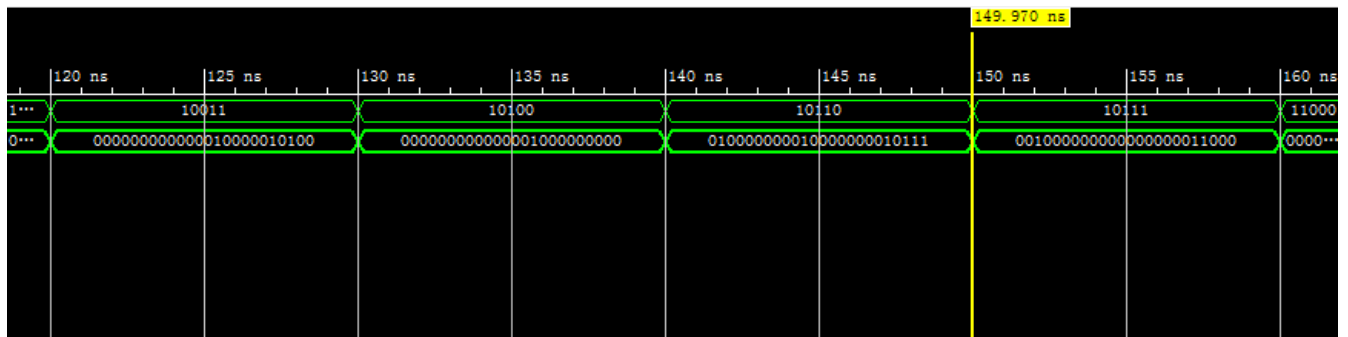


LDA

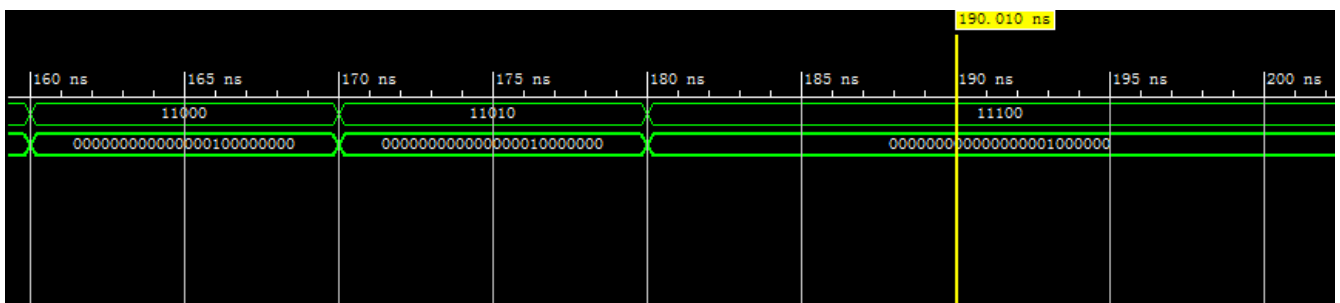

JMP


BAN

(4) CMDR

 

这里只载入了一次数据，在 25ns 处，第二行输入数据变为新值，恰逢时钟上升沿，输出改变。

(5) 总的CU

 


00H

01H

02H(跳转)

04H

 

(返回 00H)


00H

01H

02H

06H

00H

 


01H

02H

08H

00H

01H

 


02H

0AH

00H

01H

02H

 


0CH

00H

01H

02H

0EH

 

0FH

10H

00H

01H

